

# *Σχεδίαση Αναλογικών Ηλεκτρονικών Συστημάτων*


## **Βασικές Αρχιτεκτονικές PLL**

Γ. Παναγόπουλος

# Περιεχόμενα


- Analysis of Simple PLL
  - Static Behavior
  - Frequency Multiplication
  - Dynamic Behavior
  - PLL Transfer Function
  - Drawbacks of Simple PLL
- Phase/Frequency Detector
- Charge-Pump PLLs
  - Charge Pumps
  - PFD/CP/Capacitor Cascade
  - Basic Charge Pump PLL
  - PFD/CP/Capacitor Transfer Function
  - Phase Margin Calculation
- Higher-Order Loops
- Basic Charge Pump Topologies
- Settling Time
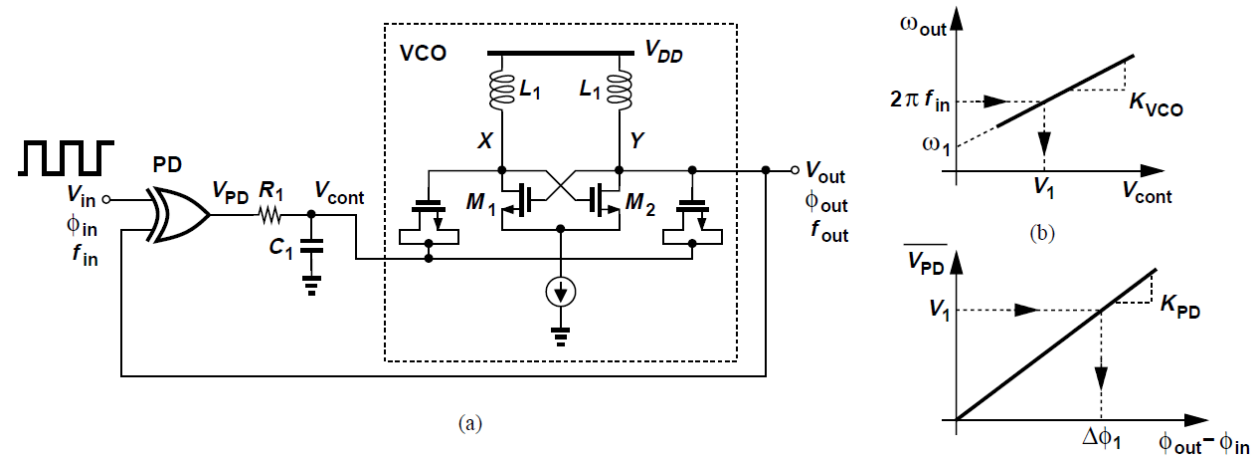
# Analysis of Simple PLL – Static Behavior




- $\Phi_{in} - \Phi_{out}$  is constant; differentiating the equation tells us that the reference and output operate at the same frequency
- To maintain a frequency  $f_{out} = f_{in}$  VCO needs a finite input voltage  $V_1$  which LPF needs to generate as the average of PD output. This translates into a finite static phase offset  $\Delta\Phi_1$  which can be undesirable based on application

# Frequency Multiplication

 


- If we wish to generate a 4GHz clock from a 20MHz reference, we can insert a frequency divider in the feedback path which is a counter which generates one pulse for every 200 input pulses
- The loop attempts to match the frequency of the output of the divider and the reference which inherently sets the output frequency to be 'M' times the reference
- This also provides programmable control over the output frequency by changing the value of M

# Dynamic Behavior – Frequency Step

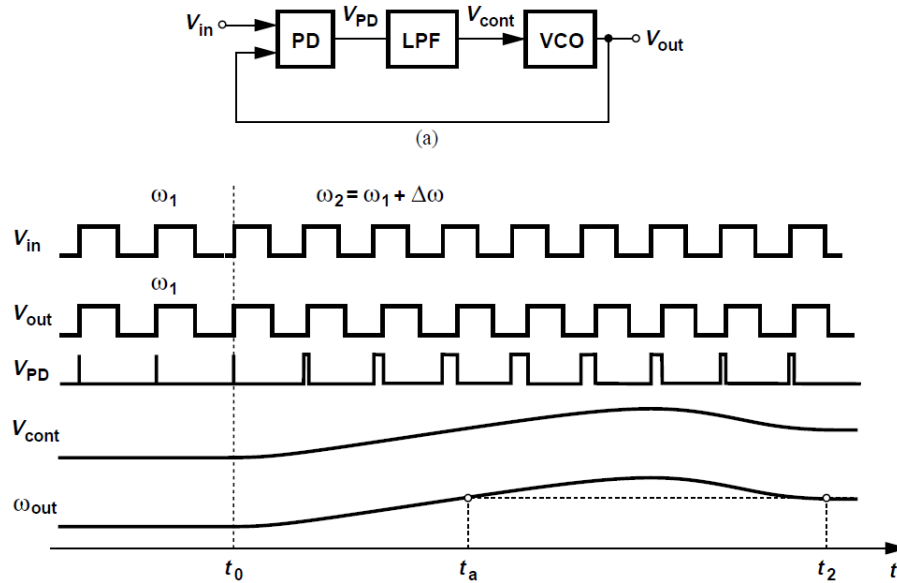

- Step the reference input voltage by  $\Delta\omega$
- The  $V_{cont}$  and  $\omega_{out}$  doesn't change immediately and phase difference grows which gradually raise  $V_{cont}$  and hence  $\omega_{out}$ ;  $\omega_{out}$  increases to new value  $\omega_2$
- To maintain the new higher frequency, higher  $V_{cont}$  and hence wider PD output pulses are required
- The exact characteristics depend on loop (example ringing if underdamped); loop not locked from  $t_a$  to  $t_2$  as phase error changes with time

# Dynamic Behavior – Phase Step

 


- Phase step is applied at  $t = t_1$
- The step immediately converts to phase error and the PD output pulses grow wider
- Consequently the  $V_{cont}$  and  $\omega_{out}$  increase and the output/feedback phase catches up to the input phase step
- The phase error and  $V_{cont}$  remain the same as before after the loop settles

# Dynamic Behavior – Remarks

- In analogy with voltage domain circuits, amplifier can only detect and correct a voltage step at its input while a PLL can do the same for a phase step and a frequency step
- The most convenient point in a PLL for monitoring transient behavior is VCO control line since other quantities are not intuitive to interpret
- Loop doesn't settle at  $t = t_a$  even though  $\omega_{out}$  is at the correct value. For locking, PLL needs both “phase acquisition” and “frequency acquisition” i.e. both  $\omega_{out}$  and  $\Delta\Phi_1$  should settle to the correct value


# PLL Transfer Function - I

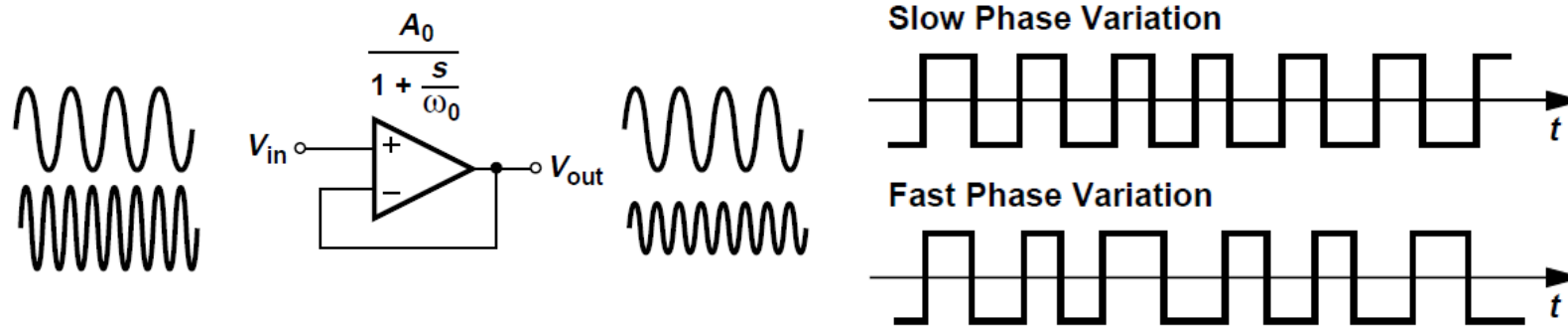

- Following the analogy with voltage domain circuits, an amplifier can follow slow changes in frequency, but it can not track too fast changes in voltage frequency of which is beyond the closed loop bandwidth; functions like LPF
- An understanding of how PLL responds to slow or fast changes in phase is desired
- Prediction: only slow phase changes are tracked



# PLL Transfer Function - II

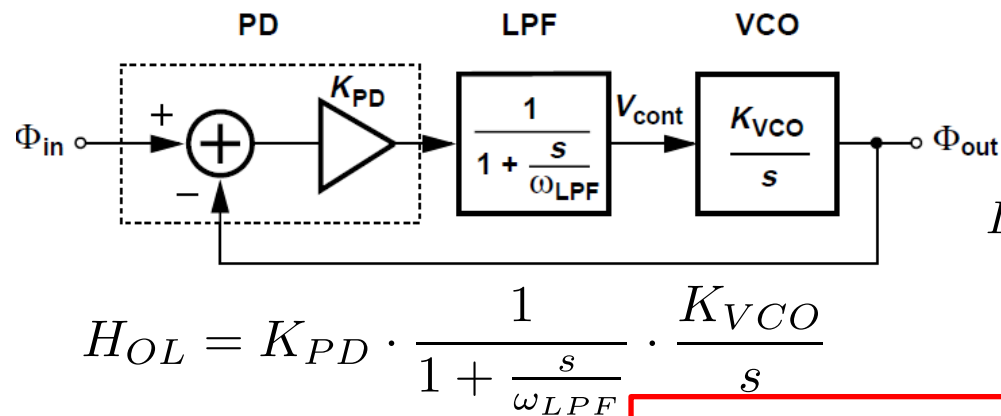

$$H_{CL}(s) = \frac{\phi_{out}(s)}{\phi_{in}(s)} = \frac{H_{OL}(s)}{1 - LG(s)}$$

$$LG(s) = -K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$

$$H_{CL}(s) = \frac{K_{PD}K_{VCO}}{s^2/\omega_{LPF} + s + K_{PD}K_{VCO}}$$

$$H_{OL} = K_{PD} \cdot \frac{1}{1 + \frac{s}{\omega_{LPF}}} \cdot \frac{K_{VCO}}{s}$$

$$H(s) = \frac{\omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}, \quad \omega_n = \sqrt{K_{PD}K_{VCO}\omega_{LPF}}$$


$$\zeta = \frac{1}{2} \sqrt{\frac{\omega_{LPF}}{K_{PD}K_{VCO}}}$$

- Blocks are replaced with their linear representation; VCO is modeled as an integrator because the output is a phase sensed by the PD
- Closed loop transfer function can be calculated
- The obtained expression is compared to the second order system general expression and damping factor ( $\zeta$ ) and natural frequency ( $\omega_n$ ) expressions are derived

# PLL Transfer Function – III

- Z informs about the stability of the loop. For critical damping, the value is  $\frac{\sqrt{2}}{2}$  ; typical value is between  $\frac{\sqrt{2}}{2}$  and 1
- The discussed topology is called “type-I” PLL because the open loop transfer function contains a single ideal integrator (one pole at origin)
- The  $\omega$  represent the rate of change of phase and not the input frequency of the loop
- For slow fluctuations, the output tracks the input variation in frequency, however, for faster input fluctuations (variation of phase at input outside loop bandwidth), the output phase fluctuations are smaller.

# PLL Transfer Function - IV

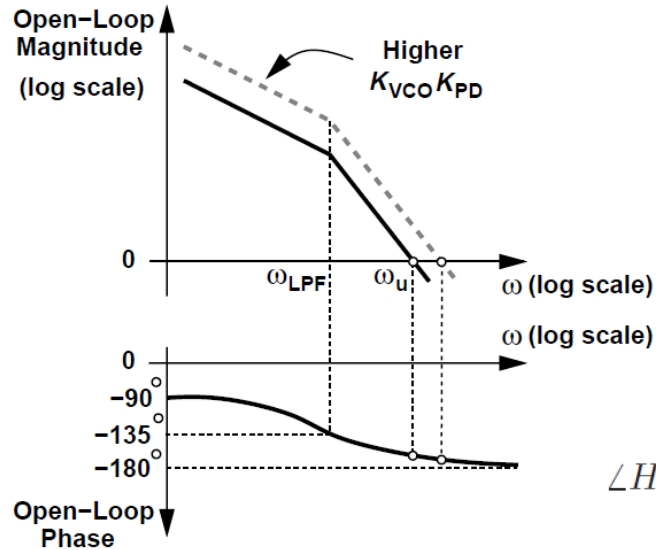

$$\frac{K_{PD}^2 K_{VCO}^2}{(1 + \frac{\omega_u^2}{\omega_{LPF}^2}) \omega_u^2} = 1$$

$$\frac{\omega_u}{\omega_{LPF}} = \sqrt{\frac{K_{PD}^2 K_{VCO}^2}{\omega_u^2} - 1}$$


$$\angle H(j\omega_u) = -90^\circ - \tan^{-1} \frac{\omega_u}{\omega_{LPF}} = -90^\circ - \tan^{-1} \sqrt{\frac{K_{PD}^2 K_{VCO}^2}{\omega_u^2} - 1}$$

- Increasing  $K_{PD}K_{VCO}$  decreases  $\zeta$ , increases gain and raises  $\omega_u$ ; phase plot is unaltered. This decreases the PM and hence stability
- $\zeta$  decreases if  $\omega_{LPF}$  is reduced thus stability is reduced if we decrease  $\omega_{LPF}$  to reduce PD injections

# Drawbacks of Simple PLL – I


- Decreasing  $\omega_{LPF}$  to reduce  $V_{cont}$  disturbances or increasing  $K_{PD}$  to reduce static phase error, both reduce the stability of the loop
- $\omega_{LPF}$  trades off with “acquisition range”, the maximum initial difference between output and reference frequency for which the loop can lock
- The loop readily fails to lock under PVT variations and other imperfections in the circuit or otherwise the performance takes a toll

# Drawbacks of Simple PLL – II

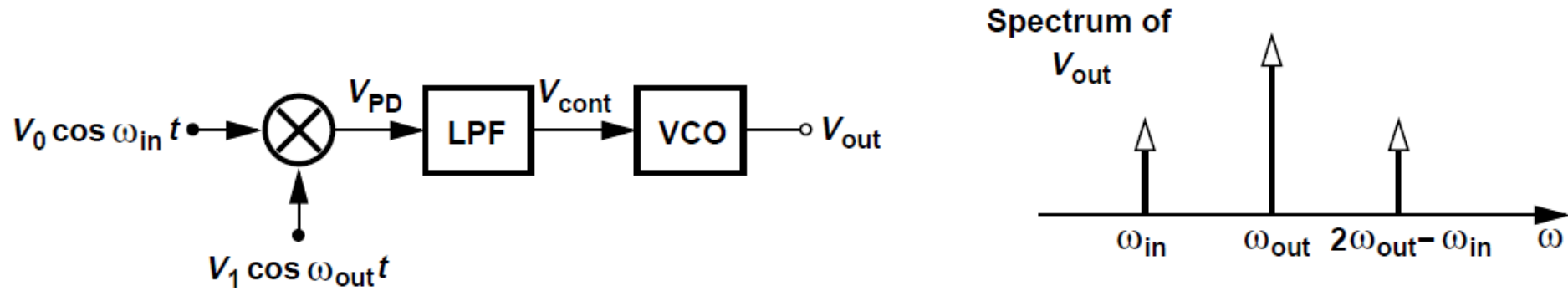


- If we take the PD to be a mixer, it generates  $\omega_{in} - \omega_{out}$  component. This is modulated by VCO to generate  $\omega_{out} \pm (\omega_{in} - \omega_{out})$  sidebands
- The band at  $\omega_{in}$  mixes at the PD to generate Dc that drives  $\omega_{out}$  towards  $\omega_{in}$
- If initial difference between  $\omega_{out}$  and  $\omega_{in}$  is large, the sideband gets more attenuated and not enough Dc can be generated, as a result the loop can not lock

# PLL using PFD

 


- PFD eliminates tradeoff between acquisition range and loop bandwidth
- PFD output is filtered and subtracted to produce  $V_{cont}$
- Type – I loop still poses trade-offs between stability, loop bandwidth and static phase error

# CP-PLLs – Charge Pump

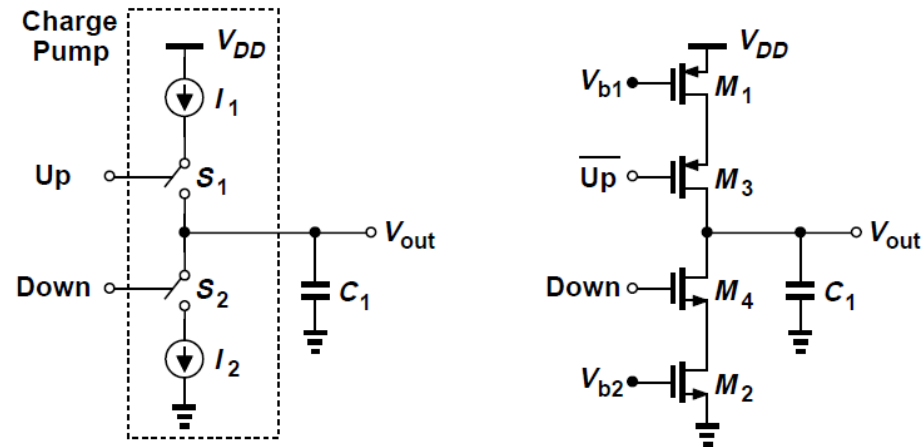

- Charge pumps (CP) are circuits which source or sink current for controlled amount of time
- $I_1$  charges  $C_1$  and  $I_2$  discharges it, given the appropriate switches are turned on
- The control signals are called Up and Down since they decide voltage of cap. rises or falls
- $I_1 = I_2 = I_p$  ; switches are placed in series with the drain of the current sources and hence this topology is called “drain-switched” CP


# CP-PLLs – PFD/CP/Capacitor Cascade

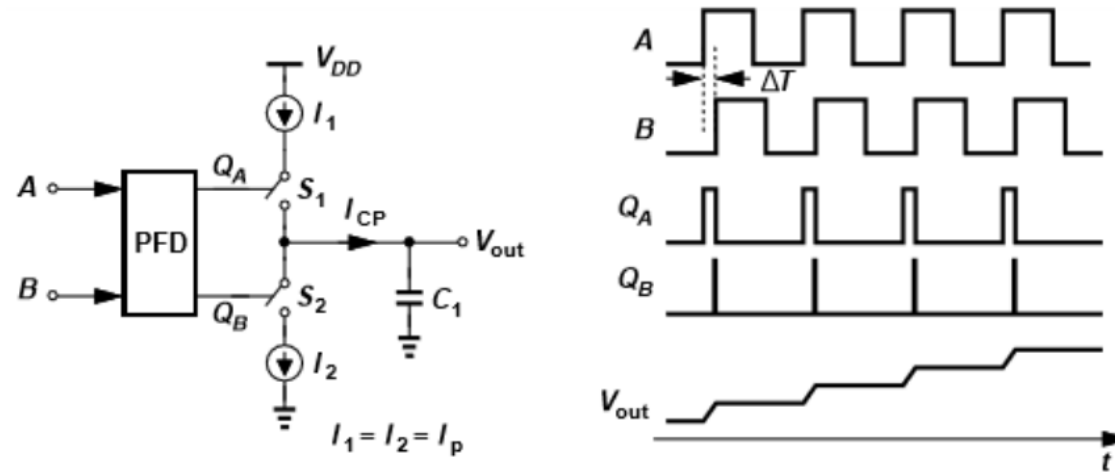

- If A and B have same frequency but finite phase error, whenever there is a comparison,  $Q_A$  goes high,  $S_1$  turns on,  $I_1$  charges  $C_1$  and  $V_{out}$  rises by  $\Delta V = (I_p/C_1)\Delta T$
- For a finite phase error,  $V_{out}$  rises indefinitely thus there is “infinite” gain
- For  $V_{out}$  to be finite, the phase error must be zero so that no net charge is injected by CP in each cycle




# CP-PLLs – Basic CP-PLL

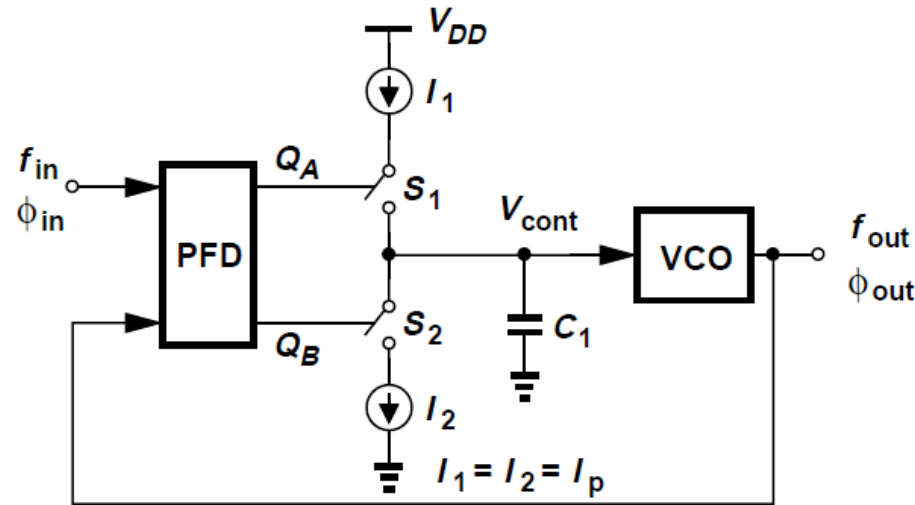


- If the loop is locked,  $f_{in} = f_{out}$  and  $V_{cont}$  has a finite value for which the CP must not inject any charge into  $C_1$  for which  $\Phi_{in} = \Phi_{out}$
- Thus, the loop locks with zero static phase error regardless of input frequency,  $K_{VCO}$  and  $I_p$
- This arises from the integration action of Charge Pump and capacitor combination

# PFD/CP/Capacitor Transfer Function - I

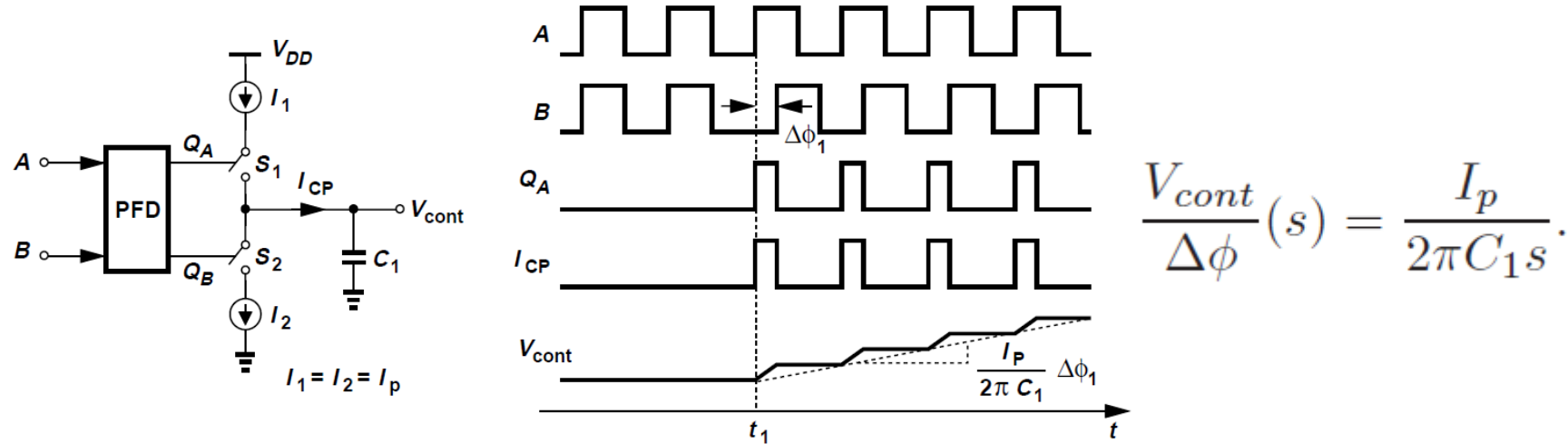

- For a phase step  $\Delta\Phi_1$  at B,  $Q_A$  remains high for  $[\Delta\phi_1/(2\pi)]T_{in}$  seconds; control voltage rises by  $\Delta V = [\Delta\phi_1/(2\pi)]T_{in}(I_p/C_1)$  at phase comparison
- The given figure is true step response of cascade; reveals that it is nonlinear since ramp slope doesn't change
- We can approximate the response by a continuous ramp with a slope of  $\Delta V/T_{in} = [\Delta\phi_1/(2\pi)](I_p/C_1)$  which suggests integration
- Thus the impulse response is  $[\Delta\phi_1/(2\pi)](I_p/C_1)u(t)$  ; the transfer function is given above
 
# PFD/CP/Capacitor Transfer Function – II





$$H(s) = \frac{I_p K_{VCO}}{2\pi C_1 s^2 + I_p K_{VCO}},$$

$$\frac{I_{CP}}{\Delta\phi}(s) = \frac{I_p}{2\pi}. \quad \text{(Equation 1)}$$

- $1/s$  signifies in the transfer function signifies pole at origin and hence an ideal integrator
- Taking the approximation one step further, we can say that the pole comes from the capacitor only and thus the transfer function of PFD/CP cascade is given by equation 1 above
- Using this we can make a linear phase model given above with open loop transfer function of  $[I_p/(2\pi C_1 s)](K_{VCO}/s)$
- The closed loop transfer function is given by  $H(s)$  and has two poles which makes loop unstable
- This architecture is called “type-II” PLL since it has two poles at origin due to the two ideal integrators

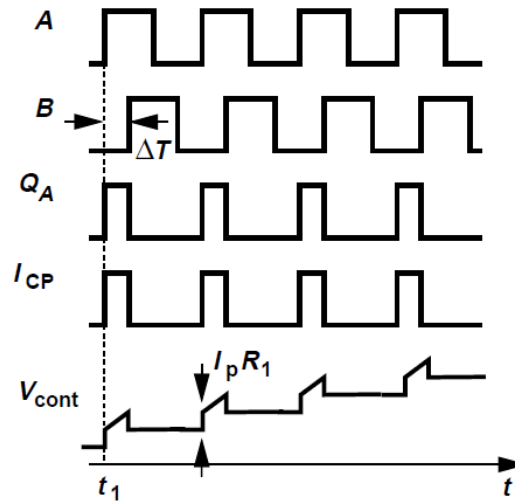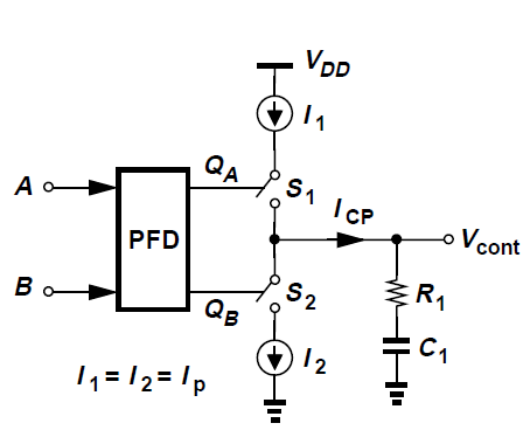
# PFD/CP/Capacitor Transfer Function – III



$$\begin{aligned} \frac{V_{cont}}{\Delta\phi}(s) &= \frac{I_{CP}}{\Delta\phi} \cdot \frac{V_{cont}}{I_{CP}} \\ &= \frac{I_p}{2\pi} \left( \frac{1}{C_1 s} + R_1 \right). \end{aligned}$$

- To make the loop stable we can either make one of the integrators lossy or introduce a zero in the loop; we pursue the latter
- A resistor  $R_1$  is placed in series with the capacitor. The control voltage abruptly jumps by  $I_p R_1$  whenever CP turns ON or OFF
- Using the same approximation as before for transfer function of PFD/CP, we get a transfer function as given above. This cascade has a zero as  $-1/(R_1 C_1)$ . The  $R_1 C_1$  branch is called “loop filter”

# Charge Pump PLL (CPPLL) – I

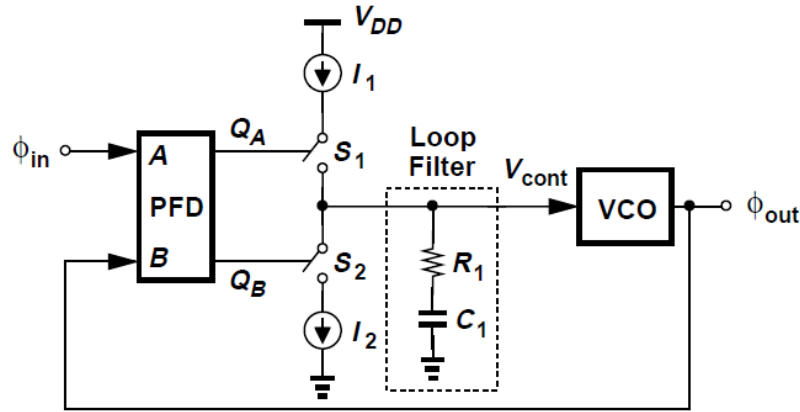



- Phase error of CPPLL is still zero
- Close loop transfer function is given by  $H(s)$
- Thus  $\omega_n$  and  $\zeta$  can be obtained
- The system exhibits low pass response (slow phase fluctuations travel to output)
- $\zeta$  increases with  $C_1$
- Architecture resolves all drawbacks of type-I PLL
- While changing  $I_p$  and  $K_{VCO}$  in opposite direction doesn't seem to have an effect on stability, too high  $K_{VCO}$  or low  $I_p$  can cause problems

$$\omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi C_1}}$$

$$\zeta = \frac{R_1}{2} \sqrt{\frac{I_p K_{VCO} C_1}{2\pi}}$$

$$H(s) = \frac{\frac{I_p K_{VCO}}{2\pi C_1} (R_1 C_1 s + 1)}{s^2 + \frac{I_p}{2\pi} K_{VCO} R_1 s + \frac{I_p K_{VCO}}{2\pi C_1}}$$

# Charge Pump PLL (CPPLL) – II

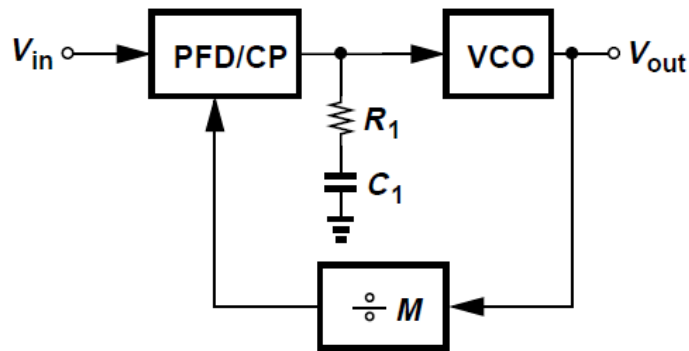 

$$\omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi C_1 M}}$$

$$\zeta = \frac{R_1}{2} \sqrt{\frac{I_p K_{VCO} C_1}{2\pi M}}$$

- Unlike type-I, CPPLL becomes more stable as  $K_{VCO}$  increases
- Higher  $K_{VCO}$  shifts up magnitude plot while not disturbing phase plot which increases  $\omega_u$  and PM
- $I_p$  has the same effect suggesting stability worse if  $I_p K_{VCO}$  falls
- For a frequency multiplication topology, effective  $K_{VCO}$  and hence stability falls
- Value of  $R_1$ ,  $I_p$ , or  $C_1$  needs to be increased to compensate for  $M$  factor
- The  $\omega_n$  and  $\zeta$  for frequency multiplying CPPLL are given

# CPPLL – Phase Margin Calculation

$$\left| \frac{I_p}{2\pi} \left( R_1 + \frac{1}{C_1 s} \right) \frac{K_{VCO}}{s} \right|_{s=j\omega_u}^2 = 1.$$

$$\left( \frac{I_p K_{VCO}}{2\pi} \right)^2 \frac{R_1^2 C_1^2 \omega_u^2 + 1}{C_1^2 \omega_u^4} = 1.$$



$$\omega_u^4 - 4\zeta^2 \omega_n^2 \omega_u^2 - \omega_n^4 = 0.$$

$$\omega_u^2 = (2\zeta^2 + \sqrt{4\zeta^4 + 1})\omega_n^2.$$

$$\begin{aligned} \text{PM} &= \tan^{-1} \frac{\omega_u}{\omega_z} \\ &= \tan^{-1} (2\zeta \sqrt{2\zeta^2 + \sqrt{4\zeta^4 + 1}}), \end{aligned}$$

- To calculate phase margin, we need to calculate frequency at which the loop gain falls to unity ( $\omega_u$ )
- The equations for  $\omega_n$  and  $\zeta$  are utilized
- Phase at  $\omega = \omega_u$  is given by zero's contribution minus  $180^\circ$  (from two poles at origin)
- Note that  $\omega_n / \omega_z = 2\zeta$
- For  $\zeta > 0.8$ ,  $\text{PM} = \tan^{-1} 4\zeta^2$
- If loop contains a divider,  $\zeta = (R_1/2) \sqrt{\frac{I_p K_{VCO} C_1}{2\pi M}}$
- Typical case:  $\zeta = 1$ ,  $\text{PM} = 76^\circ$ ,  $\omega_u / \omega_z = 4$ ;  
aggressive design:  $\zeta = \frac{\sqrt{2}}{2}$ ,  $\text{PM} = 65^\circ$ ,  $\omega_u / \omega_z = 2.2$


# Higher Order Loops – I

 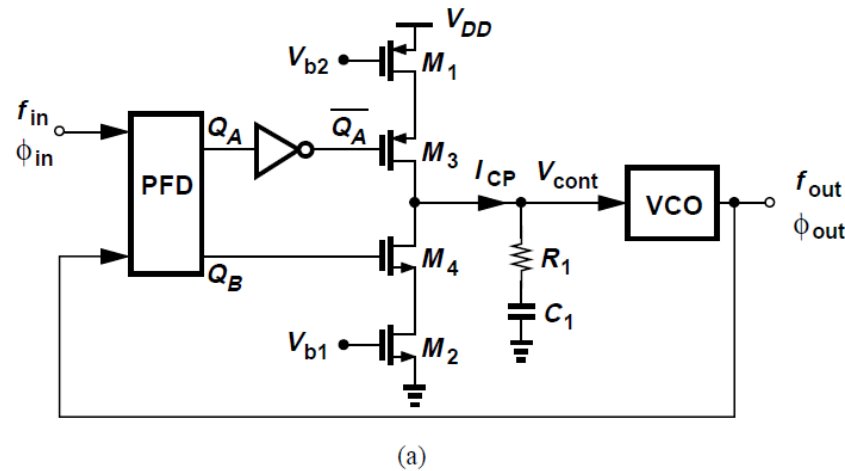

- Due to imperfections, control voltage has significant ripple
- For example if we precede  $M_3$  with an inverter to turn it ON when  $Q_A$  goes high,  $M_3$  turns on and off later than  $M_4$ : Up and Down pulses have skew
- Late turn ON: negative jump of  $I_p R_1$  and  $C_1$  slightly discharge; turn OFF: positive jump of  $I_p R_1$  and  $C_1$  charges a bit
- Can be eliminated if we interpose a pass gate between PFD and  $M_4$
- Violent jumps of the order of 8.18V on control voltage




# Higher Order Loop – II

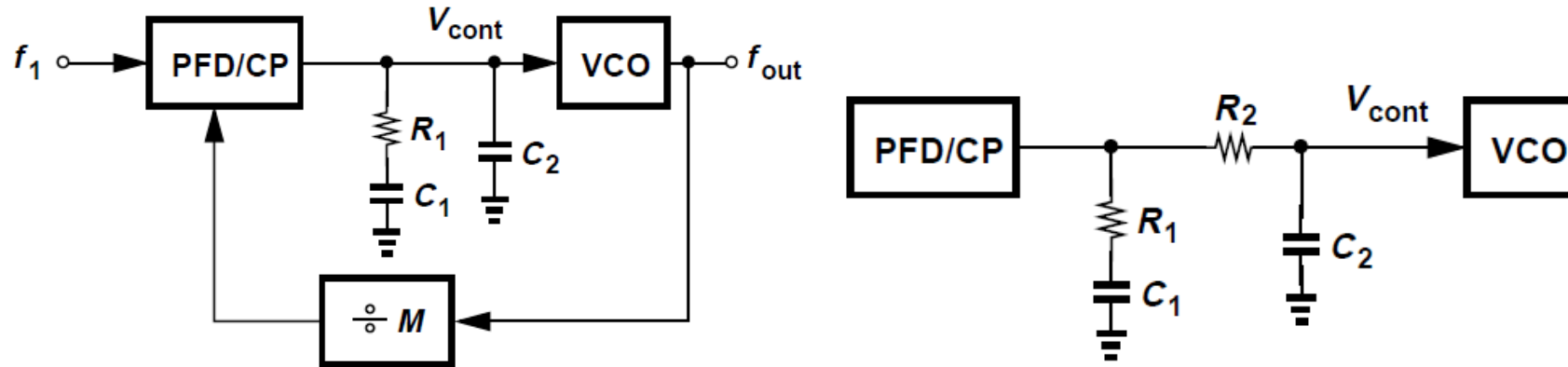


- Simple solution to problem in previous slide is to tie a capacitor between control line and ground
- Initial charge pump current flows through this capacitor reducing the ripple on control voltage
- For up/down skew, peak to peak ripple decreases to  $(I_p/C_2)T_{sk}$  which is about 1mV (for same CP current as before)
- $C_2$  raise the order of the loop to 3 and degrades PM, however,  $C_2$  as large as  $0.2C_1$  negligibly affect settling time of the loop
- Topology on right provides similar results. Voltage on  $R_1$  is allowed to jump but the second filter attenuates the ripple
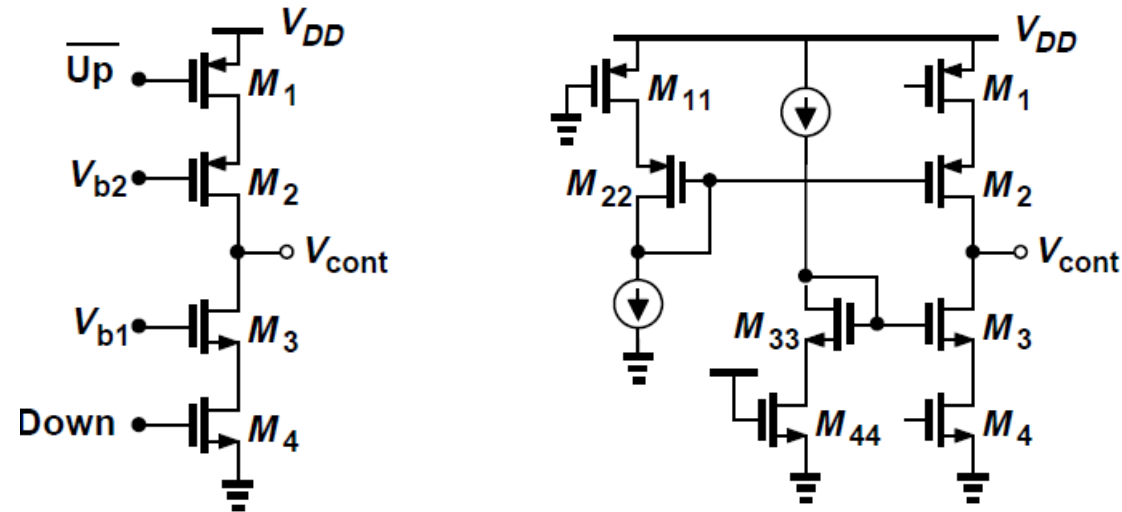
# Basic Charge Pump Topologies – Source Switched CP





- $M_3$  and  $M_2$  are current sources,  $M_1$  and  $M_4$  are switches which degenerate the former pair
- $V_{b1}$  and  $V_{b2}$  are provided by the current mirror;  $M_{44}$  and  $M_{11}$  emulate the degeneration of  $M_1$  and  $M_4$
- Due to degeneration, for given voltage headroom, output resistance is higher in this topology

# Source Switched CP – Clock Feedthrough

 

- In drain-switched topology, when  $Down$  goes from zero to  $V_{DD}$ ,  $C_{GD3}$  conducts this edge output which makes  $V_{cont}$  jump by  $V_{DD}C_{GD3}/(C_{GD3}+C_2)$
- In source-switched counterpart, the same transition will only cause node  $X$  to jump which in turn cause a jump in  $I_{D3}$  and hence no instantaneous jump in  $V_{cont}$
- $M_3$  essentially “shields” the filter from switch clock feedthrough to some extent
  
# Basic Charge Pump Topologies – Gate Switched CP



- Drain and source switched CP face voltage headroom issues due to on-resistance of the switches
- Gate-switched CP topology controls the current sources by connecting their gates to a bias voltage or to their source terminal
- Voltage range is now  $V_{DD} - |V_{GS1} - V_{TH1}| - (V_{GS2} - V_{TH2})$
- There is no charge sharing
- Drawback: skew between up and down paths => ripple on  $V_{cont}$
- M1 on when !Up falls to  $V_{DD} - |V_{TH1}| - |V_{TH5}|$ ; M2 on when Down rises to  $V_{TH2} + V_{TH6}$  => on time of M1 M2 have significant mismatch in SF and FS corners